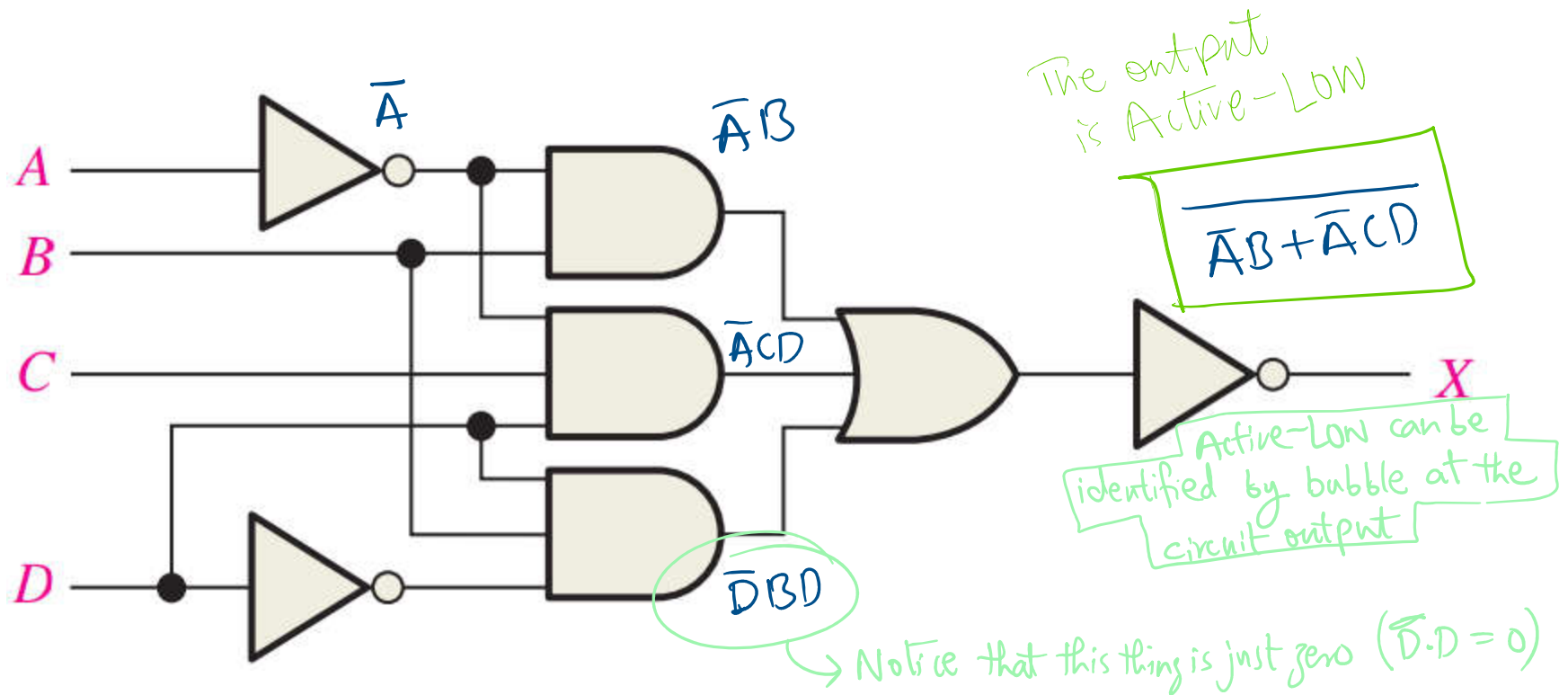


Combinational Logic / logic statements

Write the output expression for each circuit in Figure 5–54.




$$\overline{AB + \overline{A}CD} \text{ (Active low)}$$


$$0 = \overline{1} = \overline{(1)+(0)} = \overline{(0)+(1)}$$

The output is low when $\underbrace{A \text{ is low AND } B \text{ is HIGH}}_{\overline{A}B=1}$ OR $\underbrace{A \text{ is low AND } C \text{ is HIGH AND } D \text{ is HIGH}}_{\overline{A}CD=1}$

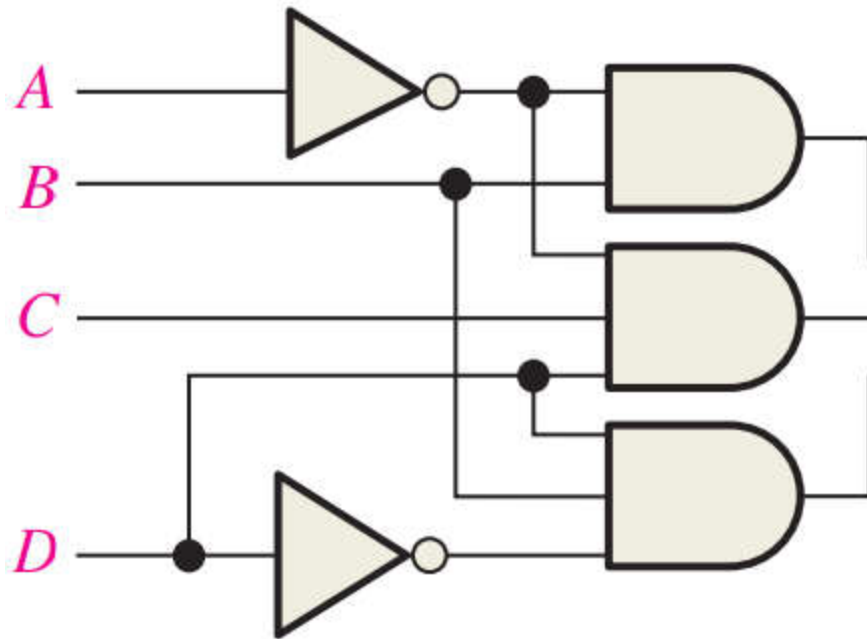To convert this circuit into Active-HIGH, use DeMorgan's theorem to eliminate the over bar in Logic Expression



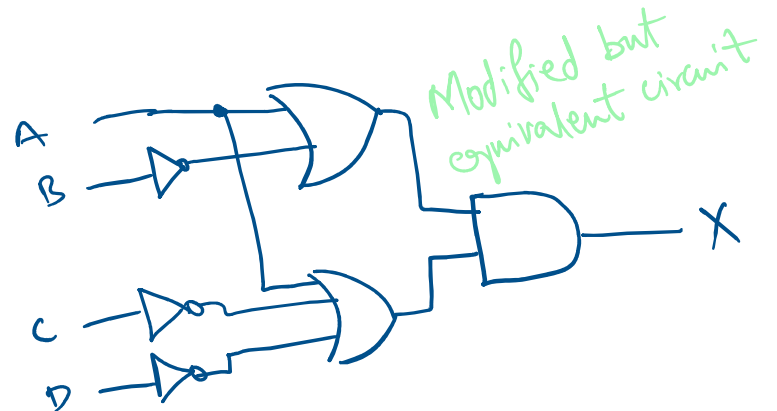
$$\overline{AB + \overline{A}CD} = \underbrace{(A + \overline{B})(A + \overline{C} + \overline{D})}_{\text{Active-HIGH}} \text{ But still their outputs (truth tables) remain the same.}$$



Combinational Logic / logic statements

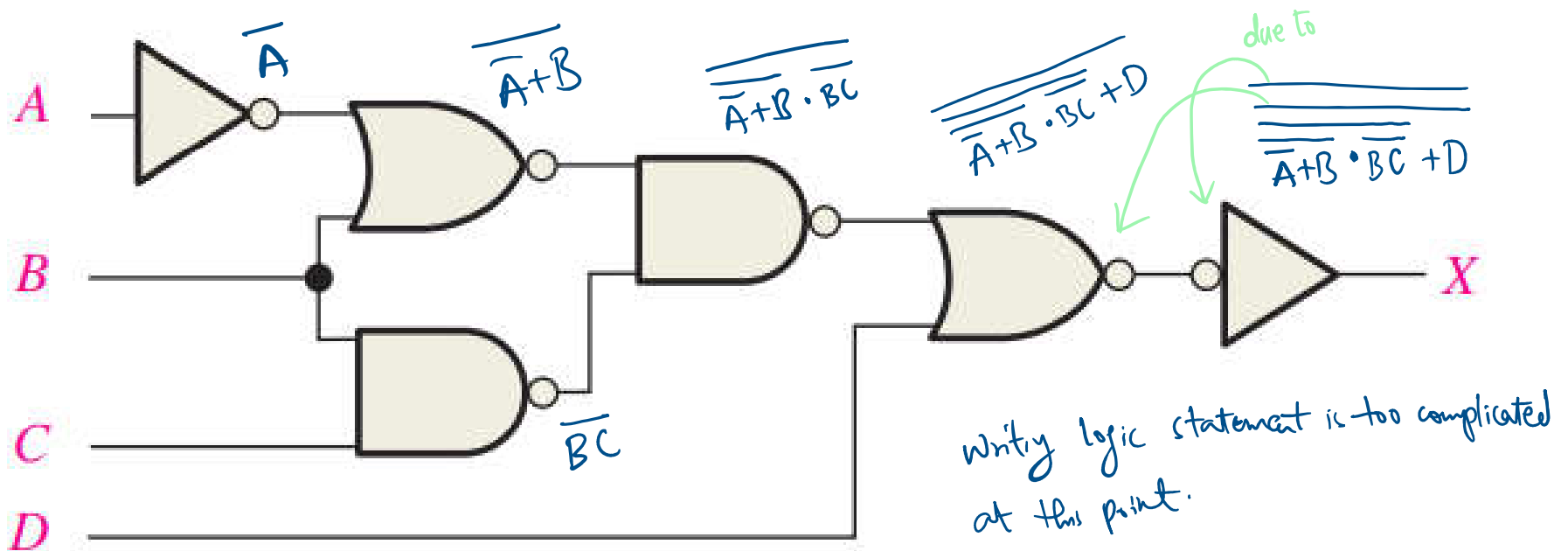Write the output expression for each circuit in Figure 5–54.



Combinational Logic / logic statements

To write logic statement we can first simplify the circuit.

1. Use Boolean Algebra
2. Use equivalent symbols

~~$$\overline{\overline{A+B \cdot BC + D}}$$~~


~~$$\overline{\overline{A+B+BC+D}}$$~~

$$\overline{A+B+BC+D}$$

$$\overline{A+B+D}$$

Active-HIGH

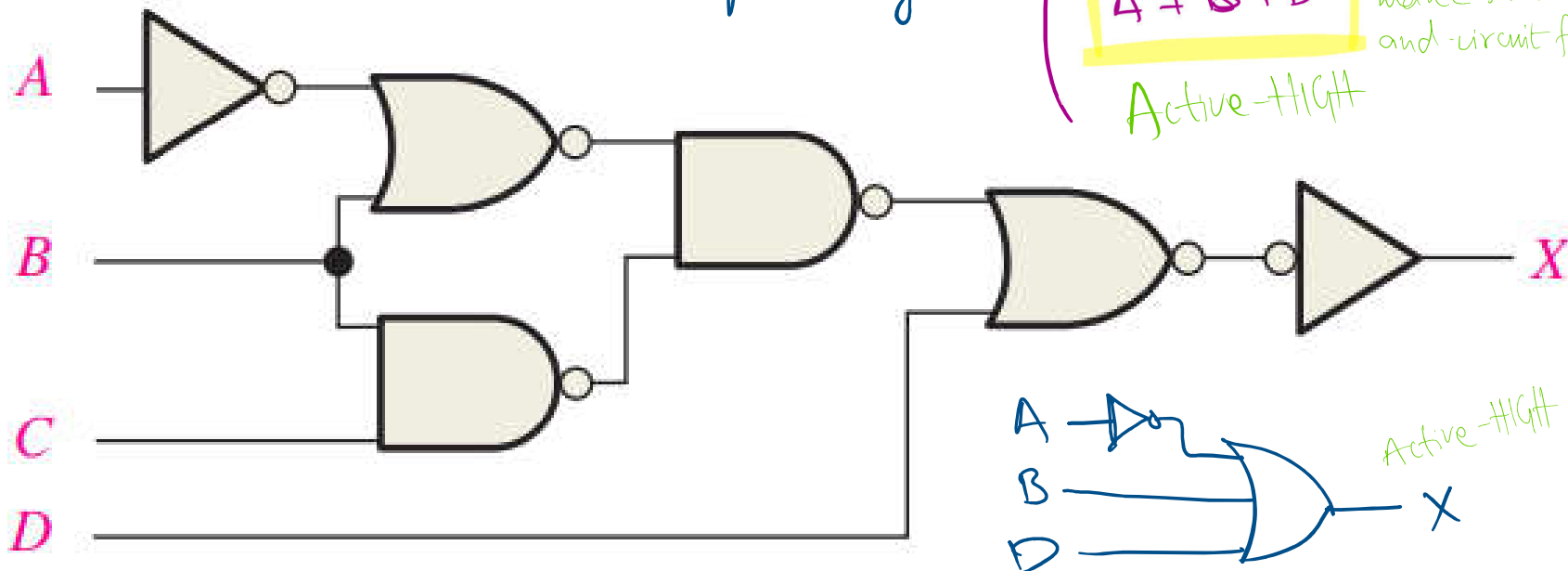much easier to make statement and circuit for




1. The output is HIGH when D is HIGH OR B is HIGH OR A is Low.

2. The output is HIGH when any of ~~D~~ B is HIGH.

Combinational Logic / logic statements

To write logic statement we can first simplify the circuit.

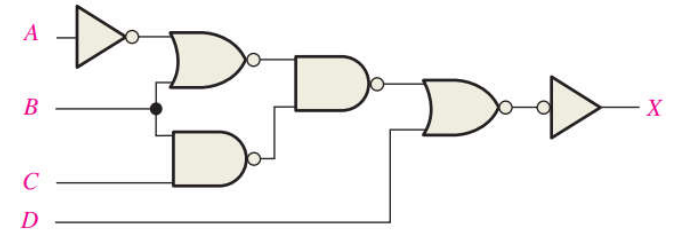
1. Use Boolean Algebra
2. Use equivalent symbols




Steps of conversion:

converted $\neg(A \wedge B) = \neg A \vee \neg B$


①

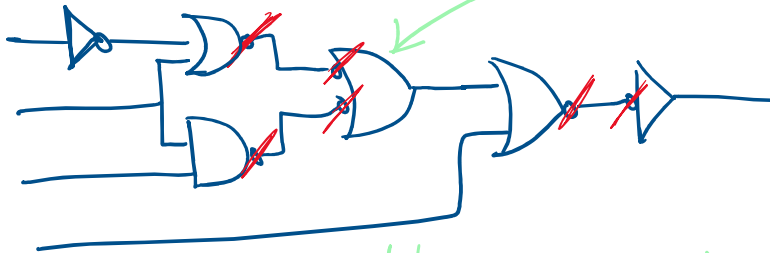


③

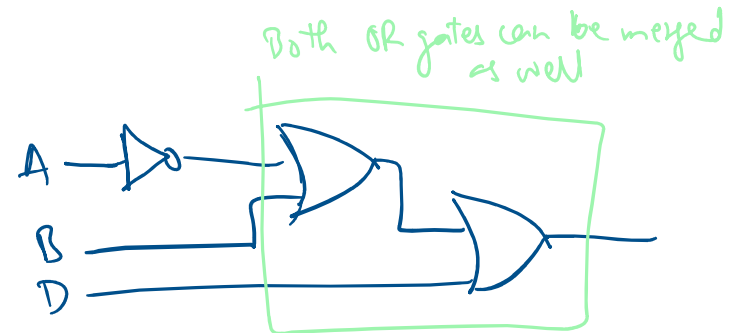

②

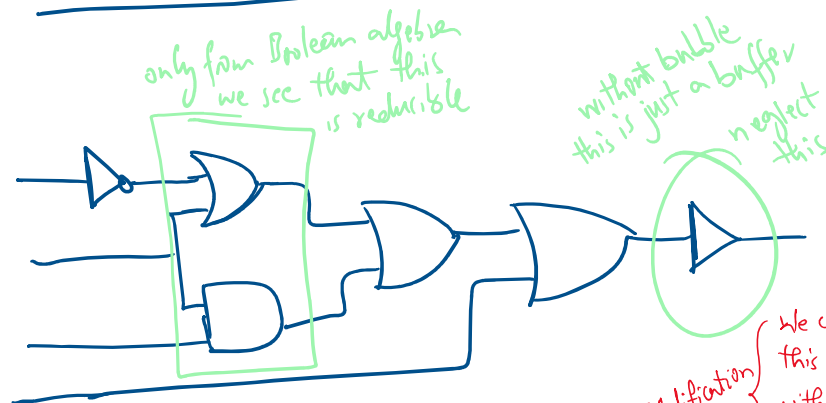

④

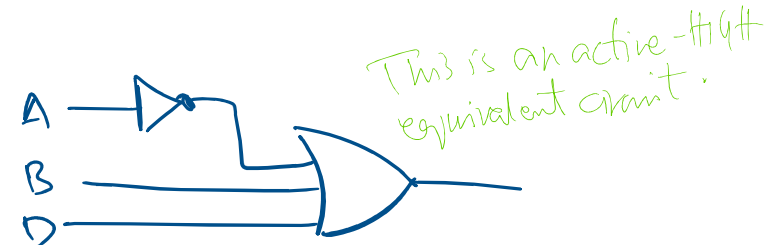

We can still convert this into Active-Low with changing the output (truth table) of the circuit.

